

MGM's
Jawaharlal Nehru Engineering College

Electrical Engineering Department

Laboratory Manual

Electric Drives

For

Final Year (EEP) Students

FOREWORD

It is my great pleasure to present this laboratory manual for Final year **ELECTRICAL ELECTRONIC & POWER** engineering students for the subject of Electric Drives. Keeping in view the vast coverage required for visualization of concepts of Electrical Drives with simple language.

As a student, many of you may be wondering with some of the questions in your mind regarding the subject and exactly what has been tried is to answer through this manual.

Faculty members are also advised that covering these aspects in initial stage itself, will greatly relieve them in future as much of the load will be taken care by the enthusiasm energies of the students once they are conceptually clear.

Dr.H.H.Shinde

Principal

INDEX

Title	Page No
1.Do's and Dont's in Laboratory	3
2 .Instruction for Laboratory Teachers:	3
3. Lab Exercises:	
1. Speed control of universal motor using scr/triac/igbt.	4
2. Speed control of DC shunt motor using chopper.	5
3. Speed control of single phase induction motor.	6
4. Speed control of three phase induction motor.	7
5. Study of closed loop speed control of AC motor.	8
6. Microcomputer based speed control of DC motor	10
7. Study of traction for trolley/ train/ bus.	11
8. Speed control of stepper motor.	13

1. DOs and DON'Ts in Laboratory:

1. Do not handle kit without reading the instructions/Instruction manuals.
2. Refer Help for Difficulties
3. Go through Manual Carefully.
4. Strictly observe the instructions given by the teacher/Lab Instructor.


2 Instruction for Laboratory Teachers:

1. Lab work completed during prior session should be corrected during the next lab session.
2. Students should be guided and helped whenever they face difficulties.
4. The promptness of submission should be encouraged by way of marking and evaluation patterns that will benefit the sincere students.

EXPERIMENT NO.:- 2

AIM: - Speed control of DC shunt motor using chopper

Circuit Diagram:-

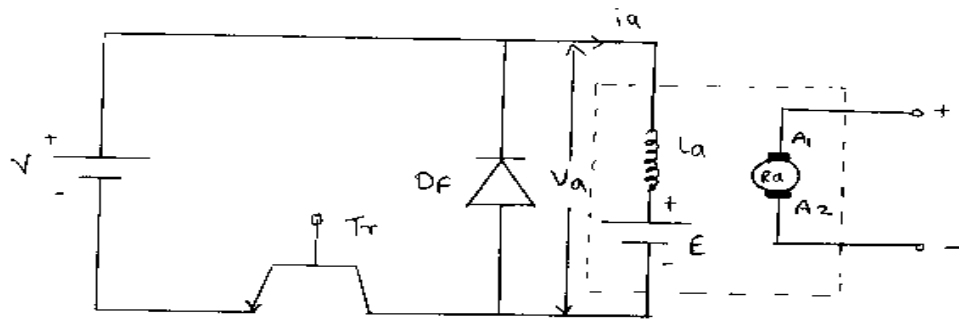

Chopper control of dc shunt excited motor

Procedure for Motoring Control:-

A transistor chopper controlled separately excited motor drive is shown in figure. Transistor Tr is operated periodically with period T and remains on for a duration Ton. Present day choppers operate at a frequency which is high enough to ensure continuous conduction.

During on period of the transistor $0 < t < t_{on}$, the the motor terminal voltage is v. The operation is described by

$$Raia + La \frac{di_a}{dt} + E = V$$

Motor operation during the interval $t_{on} < t < T$ known as freewheeling interval is described by

$$Raia + La \frac{di_a}{dt} + E = 0$$

Ratio of duty cycle t_{on} to chopper period T is called duty ratio or duty cycle (δ)

$$\delta = \text{Duty interval} / T = t_{on} / T$$

Regenerative Braking is given by

$$\delta = \text{duty interval} / T = T - t_{on} / T$$

$$W_m = \delta V / K - Rq / k^2 \cdot T$$


Output:

Conclusions:

EXPERIMENT NO.:- 3

AIM: - Speed control of single phase induction motor.

Circuit diagram:-

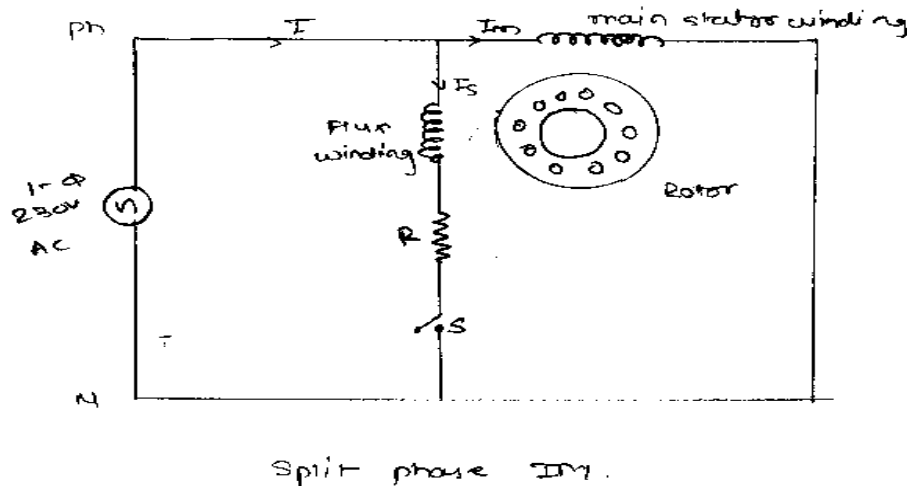

Procedure:

- 1) In split phase induction motor, the main windings have low resistance and high reactance.
- 2) These starting windings has high resistance may be increased by connecting R in series with it or by using high resistance fine copper wire for winding purpose. Hence as shown in figure the I_s drawn by starting winding lags behind the applied voltage V by a small angle whereas the I_m taken by the main windings lags V by a very large angle.
- 3) The phase angle between currents I_m and I_s is made as large as possible, because the starting torque of a split phase motor is proportional to sine of the function of centrifugal switch s is to disconnect the starting winding when gets 70-80 % of its normal running speed.
- 4) The direction of these motors can be reversed by reversing the connections of one of the two stator winding (not both).

Output:-


Conclusions:-

Conclusion:-

EXPERIMENT NO.:- 5

AIM: - Study of closed loop speed control of AC motor.

Circuit Diagram:-

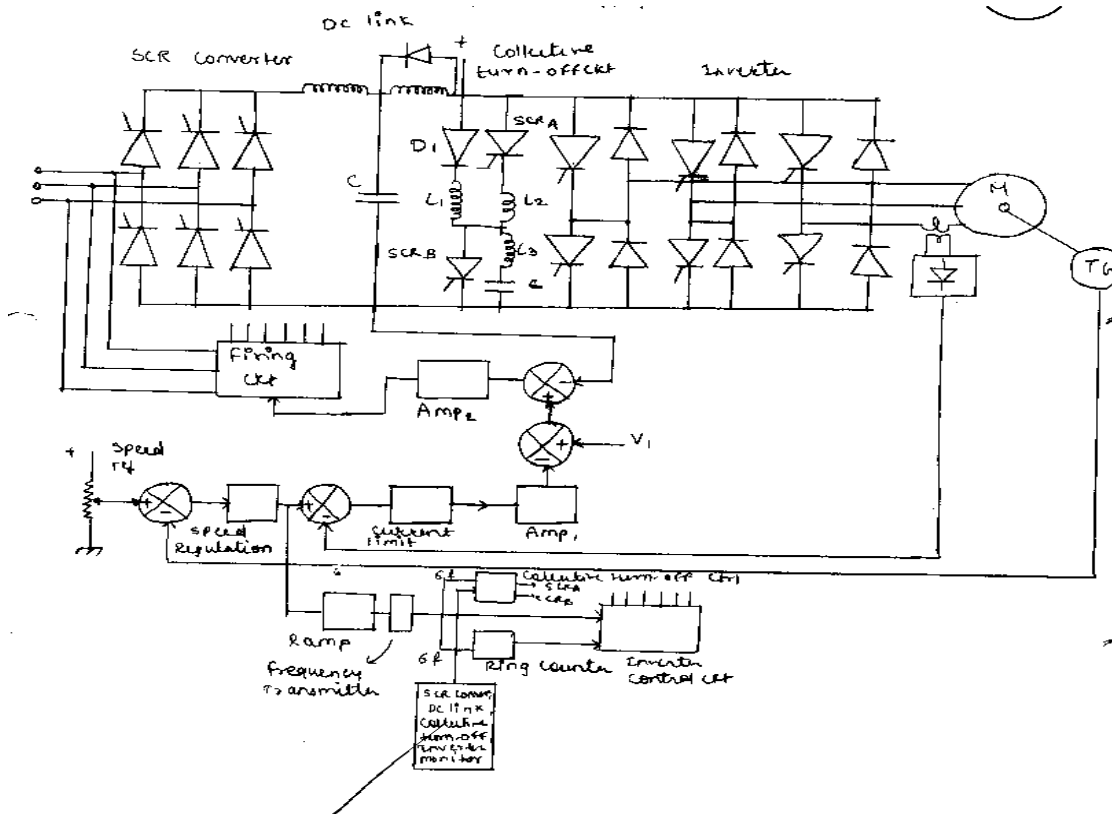

Schematic diagram of closed-loop control of variable dc link inverter for speed control of an ac motor

Theory:-

A variable voltage mode is quite satisfactory for the long term steady state operation. However if the operating conditions demand rapid acceleration and deceleration, the open loop control becomes unsatisfactory. Because the objective of the closed loop speed control system varying speed and this motor torque can be constant if rotor current and flux are kept constant.

In closed loop system it is easy to achieve the optimum operating conditions of voltage and frequency, so that the motor speed can be controlled with high torque power factor and efficiency.

In closed loop system, it is easy to monitor the air gap flux. If the rotor frequency f and the air gap flux are maintained constant if the rotor current also remains constant. Hence stator current also remains constant.

Therefore if f and ϕ are kept constant then a feedback control system, the stator current consequently remains constant developing a constant torque at all the speed of the motor. On the other hand if the stator current and air gap flux are controlled the rotor frequency automatically adjusts itself. Again if the stator current and rotor frequency then the air gap flux controlled automatically. The system in which rotor frequency controlled directly is called as controlled sub system. Schematic sine state variable frequency C link inverter with feedback control is shown in diagram. In above scheme convertor is Dc link three phase controlled rectifier.


The variable voltages are smoothed by an LC filter. An inverter is fed from a variable voltage of the convertor. The same purpose may be achieved by using uncontrolled bridge convertor in conjunction with the chopper in place of the controlled rectifier.

Conclusion:-

EXPERIMENT NO.:- 6

AIM: - Microcomputer based speed control of DC motor

Circuit Diagram:-

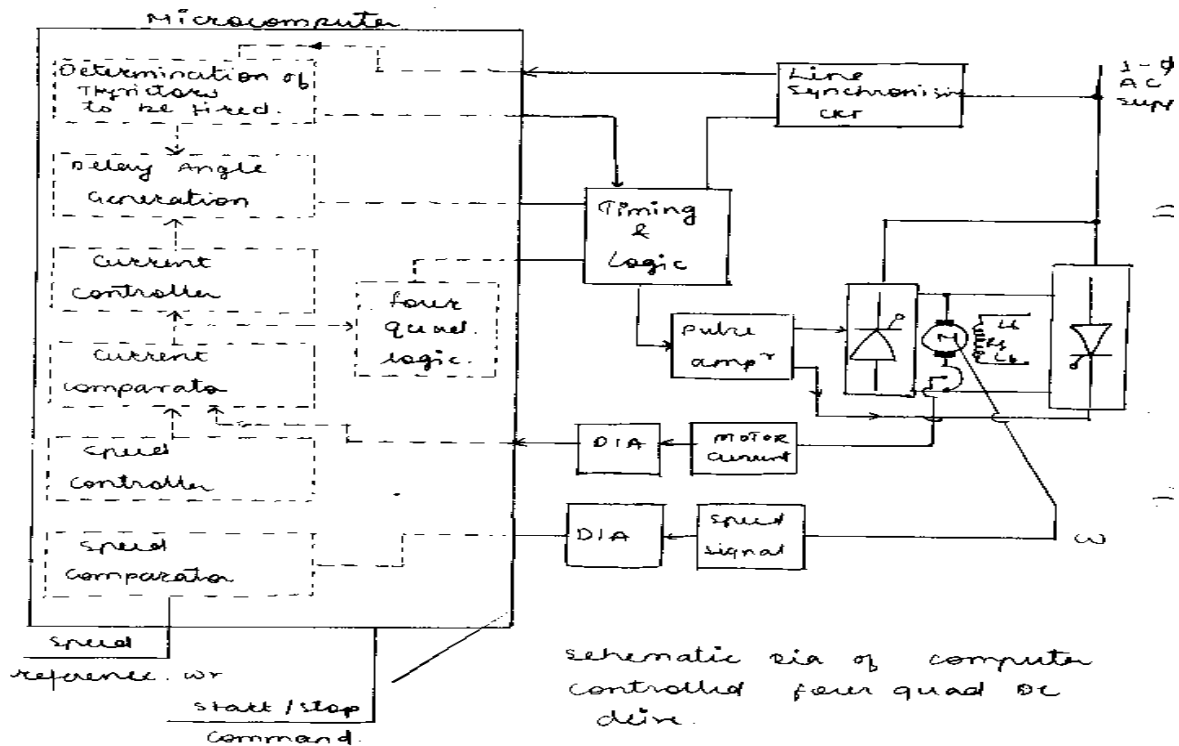

Theory:-

A microcomputer control reduces the size and cost of hardwired electronics, improving reliability and control performance. This control scheme is implemented in the software and is flexible to change the control strategy to meet different or to add extra control features.

A microcomputer control system can also perform various desirable functions. On and off of the main power supply, start and stop of the drive, speed control, current control, monitoring the control variables indicating imperfections and trip circuit, diagnostics for built in fault findings and communication with a supervisory control computer. Figure shows a schematic diagram for a microcomputer control of a convertor fed four quadrant DC drives.

The speed signal is fed into a microcomputer using an analog to digital signal convertor. To limit the armature current of the motor an inner current control is used. The armature current signal can be fed into the microcomputer through an ADC or by sampling the armature current. The line synchronizing circuit is required to synchronize the generation of the firing pulses with the supply line frequency. Although the microcomputer can perform the functions of gate pulse generator and logic circuit, these are shown outside the microcomputer. The pulse amplifier provides the necessary isolation and produces gate

pulses of required magnitude and duration. A microprocessor controlled drive has become a norm and analog control has become absolute.

Conclusion:-

EXPERIMENT NO.:- 7

AIM: - Study of traction for trolley/ train/ bus.

Circuit Diagram:-

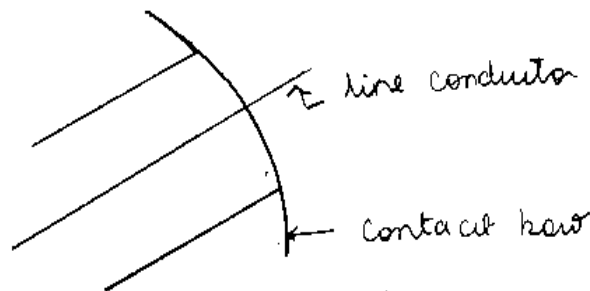


fig current collector for an electric bus.

Theory:-

Electric traction services can be broadly classified as-

- 1) Electric Trains
- 2) Electric buses, train and trolleys
- 3) Battery driven and solar powered vehicles.

A) Main Line Trains :-

Intercity passenger and goods trains which come under this category have trailer coaches carrying men and materials driven by locomotives carrying driving motors. Since driving motors travel with locomotives, power supply to the motors is arranged in two ways: From overhead transmission line is electrical locomotive and from diesel generator set mounted on the locomotive in a diesel electric locomotive.

In electric locomotive, driving motor and power modulators are housed in the locomotive. An overhead transmission line is laid along or above the track. A current collector mounted over the locomotive has a conductor strip which slides against the supply conductor and this maintain continuous contact between the supply and the locomotive. The supply conductor is commonly known as contact wire.

B) Suburban Trains:-

They are employed for transporting men within a city located at small distances. The main difference being that the distance between connective stops is much smaller for suburban trains than the main line trains. The suburban trains are also known as local trains. Because of shortage of land in cities, they are often run through underground tunnels and are called subway trains or metros or underground trains. Suburban trains are driven by motor coaches, instead of locomotives. Reason for this arrangement is

power connectivity. Each motor coach is equipped with an electric drive with its control in drives cabin and a pantograph collector. Usual pattern is to use motor coaches trailer coaches' ratio 1:2. In high speed train the ratio may be increased to 1:1.

C) Electric buses, trains and trolleys:-


Because of lower running expenses and complete absence of pollution, electric buses are preferred over diesel engine driven buses for city services and the road. As the currents are usually small, the collector consists of a rod carrying at its end a grooved wheel or two carrying at its end a grooved bridge by a contact bow collector and supply conductor. Arrangement has also to be provided for additional conductor for the returns of the current.

Conclusion:-

EXPERIMENT NO.:- 8

AIM: - Speed control of stepper motor.

Circuit Diagram:-

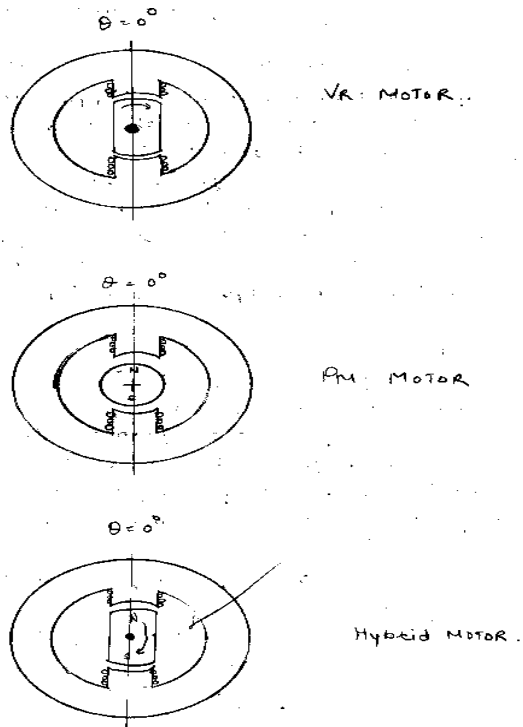

Theory:-

These motors rotate through a fixed angular step in response to each input current pulse required by its controller.

The angle through which the motor shaft rotates for each command pulse is called the step angle Beta. Smaller the step angle, greater the number of steps per revolution and higher the resolution and accuracy of positioning obtained.

Therefore Resolutions= no. Of steps / resolutions= $360 \text{ deg} / \text{beta}$

Conclusion:-